


Switches, Transistors, and Logic Gates

CS 350: Computer Organization & Assembler Language Programming

Due Tue Nov 22

 A. Why?

- Transistors (electronic switches) operate on binary data represented by voltages.
- Logic gates are the lowest level of hardware that deal with logical values.



B. Outcomes

After this lab, you should be able to


- Be able to read and write simple voltage/current diagrams, transistor-level diagrams, and logic gates-level diagrams.
- Convert between truth tables, logical formulas, and loop-free logic circuits.

C. Problems [50 points total]

①

X	Y	Z	W
0	0	0	1
0	0	1	1
0	1	0	Short
0	1	1	0
1	0	0	Short
1	0	1	0
1	1	0	Short
1	1	1	0

 
- [16 pts] Study the voltage diagram shown here. Give a table that maps shows (for each configuration of inputs X, Y, and Z): Is power is connected to output W? Is W is connected to ground? What's the status of the circuit? (W = 0 or 1 or we have a short or open circuit?) See the table at the top of page 7 of Lecture 15 for an example.




- [6 pts] Modify the voltage diagram for Problem 1 to get a proper CMOS circuit that calculates $W = \overline{X} \overline{Y} + \overline{Z}$. Don't modify the p-type transistors. Instead, add / remove / rewrite n-type transistors for X, Y, and Z as necessary.
- [13 pts] Draw a transistor-level circuit for $Z = \overline{A}(\overline{B} + \overline{C})\overline{D}$. Be sure to (a) use p-type transistors to connect output Z to power iff $\overline{A}(\overline{B} + \overline{C})\overline{D}$ is true and (b) use n-type transistors to connect Z to ground iff $\overline{A}(\overline{B} + \overline{C})\overline{D}$ is false.

2) $W = \bar{X} \cdot \bar{Y} + \bar{Z}$
aka

$(\bar{X} \wedge \bar{Y}) \vee \bar{Z}$

 


x	y	z	w
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

 

(as p-type)

X	Y	Z	W
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

a	b	c	d	z
0	?	?	?	0
0	?	?	?	0
?	?	?	?	1
0	0	1	0	0
0	0	0	0	0
0	0	0	1	0
0	1	1	1	0

 


3) $Z = \bar{A}(\bar{B} + \bar{C})\bar{D}$

Use p-type to connect $Z \rightarrow -$ iff $Z = 1$

Use n-type to connect $Z \rightarrow +$ iff $Z = 0$

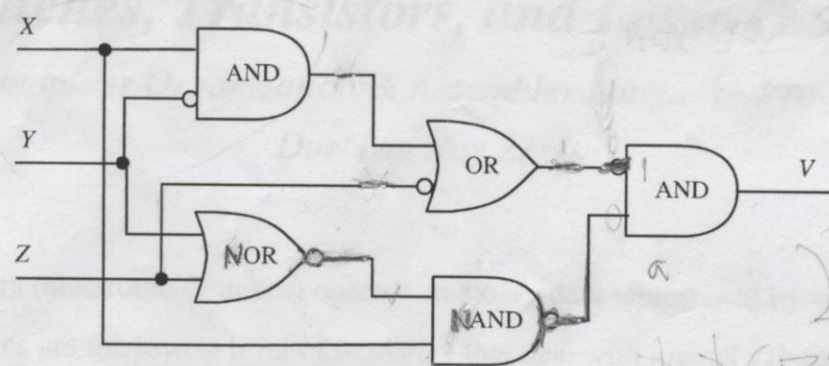4. [15 = 3*5 pts] Consider the circuit below with inputs X, Y, Z and output V .



- (a) Translate the logic circuit to get a boolean expression definition for V . Give the expression as is (don't manipulate it and give something logically equivalent).
 Notation: You can use \otimes and \oplus for *NAND* and *NOR* (or write them as the *NOT* of an *AND* or *OR*; your choice). You can also use juxtapositioning, \wedge , or $*$ for *AND* and \vee or $+$ for *OR* (your choice).
- (b) Give a truth table for V (either style of table is okay).
- (c) Give the full DNF definition for V . Use it to draw a PLA-based logic circuit for V . (Feel free to drop unused AND gates, but keep 3 inputs per AND gate.)

X	Y	Z	V
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0

$$\neg((X \wedge \bar{Y}) \vee \bar{Z}) \wedge \neg(\neg(Z \vee Y) \bar{X})$$

$$\neg((X \wedge \bar{Y}) \vee \bar{Z}) \wedge \neg((Z \vee Y) \bar{X})$$

$$\dots \wedge \neg((Z \vee Y) \wedge X)$$


$$\neg \neg(Z \vee Y)$$

$$\boxed{((X \wedge \bar{Y}) \vee \bar{Z}) \wedge (X \wedge (Z \vee Y))} = Z \vee Y$$

$$\neg((X \wedge \bar{Y}) \vee \bar{Z}) \wedge ((Z \vee Y) \bar{X}) \quad (X)$$

$$(X \wedge \bar{Y} \wedge Z) \vee (Y \wedge \bar{Z}) \vee (\bar{Z} \wedge \bar{X})$$

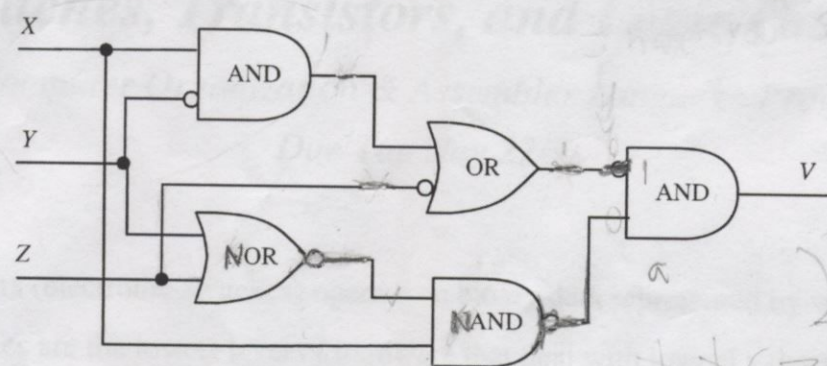4. [15 = 3*5 pts] Consider the circuit below with inputs X, Y, Z and output V .



- (a) Translate the logic circuit to get a boolean expression definition for V . Give the expression as is (don't manipulate it and give something logically equivalent).
Notation: You can use \otimes and \oplus for *NAND* and *NOR* (or write them as the *NOT* of an *AND* or *OR*; your choice). You can also use juxtapositioning, \wedge , or $*$ for *AND* and \vee or $+$ for *OR* (your choice).
- (b) Give a truth table for V (either style of table is okay).
- (c) Give the full DNF definition for V . Use it to draw a PLA-based logic circuit for V . (Feel free to drop unused AND gates, but keep 3 inputs per AND gate.)

X	Y	Z	V
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0

$$\neg((X \wedge \bar{Y}) \vee \bar{Z}) \wedge \neg(\neg(Z \vee Y) \bar{X})$$

$$\neg((X \wedge \bar{Y}) \vee \bar{Z}) \wedge \neg((Z \vee Y) \bar{X})$$

$$\dots \wedge \neg((Z \vee Y) \wedge X)$$


$$\neg \neg(Z \vee Y)$$

$$\boxed{((X \wedge \bar{Y}) \vee \bar{Z}) \wedge (X \wedge (Z \vee Y))} = Z \vee Y$$

$$\neg((X \wedge \bar{Y}) \vee \bar{Z}) \wedge ((Z \vee Y) \wedge X) \quad (X)$$

$$(X \wedge \bar{Y} \wedge Z) \vee (Y \wedge \bar{Z}) \vee (\bar{Z} \wedge \bar{X})$$

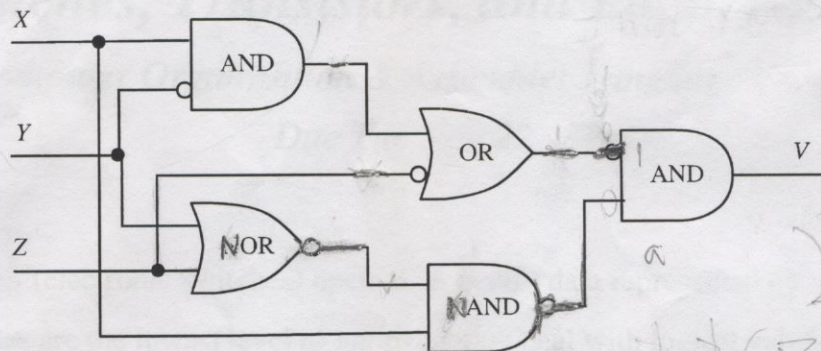4. [15 = 3*5 pts] Consider the circuit below with inputs X, Y, Z and output V.



- (a) Translate the logic circuit to get a boolean expression definition for V. Give the expression as is (don't manipulate it and give something logically equivalent). Notation: You can use \otimes and \oplus for *NAND* and *NOR* (or write them as the *NOT* of an *AND* or *OR*; your choice). You can also use juxtapositioning, \wedge , or $*$ for *AND* and \vee or $+$ for *OR* (your choice).
- (b) Give a truth table for V (either style of table is okay).
- (c) Give the full DNF definition for V. Use it to draw a PLA-based logic circuit for V. (Feel free to drop unused AND gates, but keep 3 inputs per AND gate.)

X	Y	Z	V
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0

$$\neg((X \wedge \bar{Y}) \vee \bar{Z}) \wedge \neg(\neg(Z \vee Y) \wedge X)$$

$$\neg((X \wedge \bar{Y}) \vee \bar{Z}) \wedge \neg((Z \vee Y) \wedge X)$$

$$((X \wedge \bar{Y}) \vee \bar{Z}) \wedge (X \wedge \neg(Z \vee Y))$$

$$\neg \neg(Z \vee Y) = Z \vee Y$$

$$\neg((X \wedge \bar{Y}) \vee \bar{Z}) \wedge ((Z \vee Y) \wedge X) \quad (X)$$

$$(X \wedge \bar{Y} \wedge Z) \vee (Y \wedge \bar{Z}) \vee (\bar{Z} \wedge X)$$