

*Johnny post*

# Combinatorial Circuits; Storage Elements

CS 350: Computer Organization & Assembler Language Programming

Due Tue Nov 29 (no late assignments)

## A. Why?

- Combinatorial logic circuits correspond to pure (state-free) calculations on booleans.
- Storage elements are the basic circuits that store data.

## B. Outcomes

After this lab you should be able to

- Translate between simple combinatorial logic circuits and boolean expressions.
- Recognize whether a circuit can be said to remember or store data.
- Describe how R-S and D latches work as storage elements

## C. Problems [50 points total]


$X_i$	$T_i$	$Y_i$	$T_{i+1}$
0	0	1	0
0	1	0	0
1	0	0	0
1	1	1	0

1. [14 = 7 + 7 pts] Let's implement 2's complement negative ( $Y = -X$ ) using a modular design. At position  $i$ , we have bit  $Y_i = \overline{X}_i$  or  $Y_i = X_i$  depending on whether bit  $X_i$  is or is not in the trailing (i.e., rightmost) 10...0 section of  $X$ . Let  $T_i = 1$  if position  $i$  contains a rightmost zero or is the 1 bit just before the rightmost zeros, and let  $T_i = 0$  otherwise. Note  $T_0$  always = 1.

- Give equations for outputs  $Y_i$  and  $T_{i+1}$  from inputs  $X_i$  and  $T_i$ .
- Give logic gate implementations of  $Y_i$  and  $T_{i+1}$  using inputs  $X_i$  and  $T_i$ . You can give a PLA-based implementation or you can simplify using any/all of the standard gates (AND, OR, NAND, NOR, XOR, XNOR, and NOT), your choice.

1a)  $Y_i = \overline{X_i} \vee T_i$

$T_{i+1} = \overline{X_i} \wedge T_i$

 




2. [16 = 4 + 4 + 4 + 6 pts] Consider the following partial statements about  $R$ - $S$  latches. Map each of (a) – (d) to all of (1) – (5) that apply.

- $Q_{n+1} = d_n$  →
- |   |   |
|---|---|
| (a) If $RS$ then ...                            | (1) $Q = 01$ is stable                              |
| (b) If $\bar{R}S$ then ... <u>1, 5</u>          | (2) $Q = 10$ is stable                              |
| (c) If $R\bar{S}$ then ... <u>2, 4</u>          | (3) $Q = 11$ is stable                              |
| (d) If $\bar{R}\bar{S}$ then ... <u>3, 6, 7</u> | (4) If $Q = 01$ then $Q = 11$ then 10 and is stable |
|   | (5) If $Q = 10$ then $Q = 11$ then 01 and is stable |
|   | (6) If $Q = 01$ then $Q = 11$ and is stable         |
|   | (7) If $Q = 10$ then $Q = 11$ and is stable         |

3. [18 = 4 + 6 + 4 + 4 pts] Study this logic circuit.

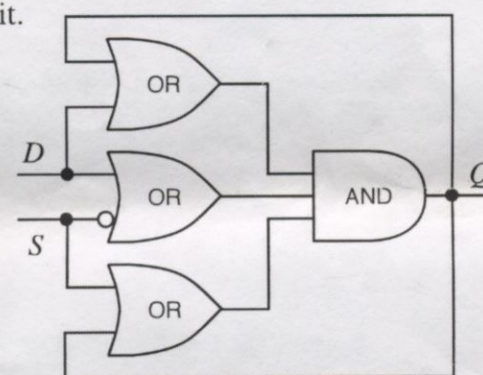- a. Translate the circuit to an equation for new  $Q$  = a boolean expression over  $D$ ,  $S$ , and (the current value of)  $Q$ . (Make the translation direct.)
- b. Simplify your equation from part (a) to get new  $Q$  = a DNF expression. (Doesn't have to be full DNF.) Show your work.
- c. When does this circuit have logically stable or unstable values for  $Q$ ?
- d. How this circuit be used to store a bit? I.e., how can we set / reset / maintain the value of  $Q$ ?



b)  $Q = (d \wedge s) \vee \neg Q$

a)  $Q = (Q \vee D) \wedge (D \vee \neg S) \wedge (S \vee Q)$

c) when

d)  $Q$  can be set if  $(d \text{ and } s) = 1$ .  
 $Q$  gets reset to 0 if  $(s \text{ not } 1) \text{ and } (s = 1) \text{ and } (d = 0)$




2. [16 = 4 + 4 + 4 + 6 pts] Consider the following partial statements about R-S latches. Map each of (a) – (d) to all of (1) – (5) that apply.

- $+3 = d_n$  → (a) If  $RS$  then ... (1)  $Q = 01$  is stable  
 (b) If  $\overline{R}S$  then ... 1, 5 (2)  $Q = 10$  is stable  
 (c) If  $R\overline{S}$  then ... 2, 7 (3)  $Q = 11$  is stable  
 (d) If  $\overline{R}\overline{S}$  then ... 3, 6, 7 (4) If  $Q = 01$  then  $Q = 11$  then 10 and is stable  
 (5) If  $Q = 10$  then  $Q = 11$  then 01 and is stable  
 (6) If  $Q = 01$  then  $Q = 11$  and is stable  
 (7) If  $Q = 10$  then  $Q = 11$  and is stable

3. [18 = 4 + 6 + 4 + 4 pts] Study this logic circuit.

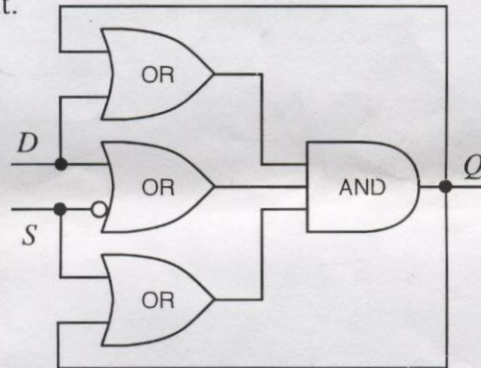- a. Translate the circuit to an equation for new  $Q =$  a boolean expression over  $D$ ,  $S$ , and (the current value of)  $Q$ . (Make the translation direct.)
- b. Simplify your equation from part (a) to get new  $Q =$  a DNF expression. (Doesn't have to be full DNF.) Show your work.
- c. When does this circuit have logically stable or unstable values for  $Q$ ?
- d. How this circuit be used to store a bit? I.e., how can we set / reset / maintain the value of  $Q$ ?



$$(d \wedge s) \vee \neg Q$$

$$Q = (Q \vee D) \wedge (D \vee \neg S) \wedge (S \vee Q)$$

Q can be set if  $(d \text{ and } s) = 1$ .  
 Q gets reset to 0 if  $(s = 1)$  and  $(d = 0)$